

Experiment No. 3

Page:

Date:

Object \Rightarrow To plot output and transfer characteristic of FET

Apparatus used \Rightarrow FET, D.C. Voltmeter, D.C. milliammeter, D.C. power supply.

Circuit \div Circuit shown in figure. G is the Gate. D is the Drain, and S is source etc.

observation

Table for output characteristic

| Ser. N. | $V_{GS} = -1V$ | | $V_{GS} = -2V$ | | $V_{GS} = -3V$ | |
|---------|--------------------|---------------|--------------------|---------------|--------------------|---------------|
| | V_{DS} (Volt) | I_D (mA) | V_{DS} (Volt) | I_D (mA) | V_{DS} (Volt) | I_D (mA) |
| 1 | 1 | 3.8 | 1 | 2.6 | 1 | 1.2 |
| 2 | 2 | 5.4 | 2 | 3.4 | 2 | 1.8 |
| 3 | 3 | 6.2 | 3 | 4.2 | 3 | 1.8 |
| 4 | 4 | 6.2 | 4 | 4.2 | 4 | 1.8 |

Calculations: From Graph

Drain resistance

$$r_{d} = \left(\frac{\Delta V_{DS}}{\Delta I_D} \right)_{V_{GS}}$$

$$= \frac{3.5 - 15}{(6.7 - 4.7) \times 10^{-3}}$$

$$= \frac{210}{1.5} \times 10^3 = 4/5 \times 10^5 \text{ ohms}$$

$$r_{d} = 0.8 \times 10^8 \Omega$$

$$g_m = \left(\frac{\Delta I_D}{\Delta V_{GS}} \right)_{V_{DS}}$$

$$= \frac{7.4 - 18}{-2.7}$$

$$= 2.2 \text{ } \Omega^{-1}$$

$$\mu = g_m \times r_{d}$$

$$= 2.2 \times 0.8 \times 10^8$$

$$\mu = 1.76 \times 10^8$$

Table for Transfer characteristic

| Ser No | $V_{GS} = 3V$ | |
|--------|-----------------|------------|
| | V_{GS} (Volt) | I_D (mA) |
| 1 | 0 | 10 |
| 2 | -1 | 6.8 |
| 3 | -2 | 4.0 |
| 4 | -3 | 1.8 |
| 5 | -4 | 0.6 |
| 6 | -5 | 0.0 |

Result \Rightarrow In the graph

pitch of Voltage = -5 Volt

Drain resistance (r_{d}) = $0.8 \times 10^8 \Omega$

$g_m = 2.2 \Omega^{-1}$ $\mu = 1.76 \times 10^8$

Precaution \Rightarrow

- (1) Handle FET Gently
- (2) Gate should be given a +ve Voltage
- (3) Voltage being applied should not exceed the stated values.